

The first step in this project is to design a simple LED circuit. Then we will make the LED circuit controllable from the Raspberry Pi by connecting the circuit to the general purpose input/output (GPIO) pins on the Raspberry Pi.

A simple LED circuit consists of a LED and resistor. The resistor is used to limit the current that is being drawn and is called a *current limiting resistor*. Without the resistor the LED would run at too high of a voltage, resulting in too much current being drawn which in turn would instantly burn the LED, and likely also the GPIO port on the Raspberry Pi.


To calculate the resistor value we need to examine the specifications of the LED. Specifically we need to find the forward voltage (VF) and the forward current (IF). A regular red LED has a forward voltage (VF) of 1.7V and forward current of 20mA (IF). Additionally we need to know the output voltage of the Raspberry Pi which is 3.3V.

We can then calculate the resistor size needed to limit the current to the LED's maximum forward current (IF) using ohm's law like this:

$$[R_{\Omega} = \frac{V}{I} = \frac{3.3 - V_F}{I_F} = \frac{3.3 - 1.7}{20 \text{ mA}} = 80 \Omega]$$

Unfortunately 80 ohm is not a standard size of a resistor. To solve this we can either combine

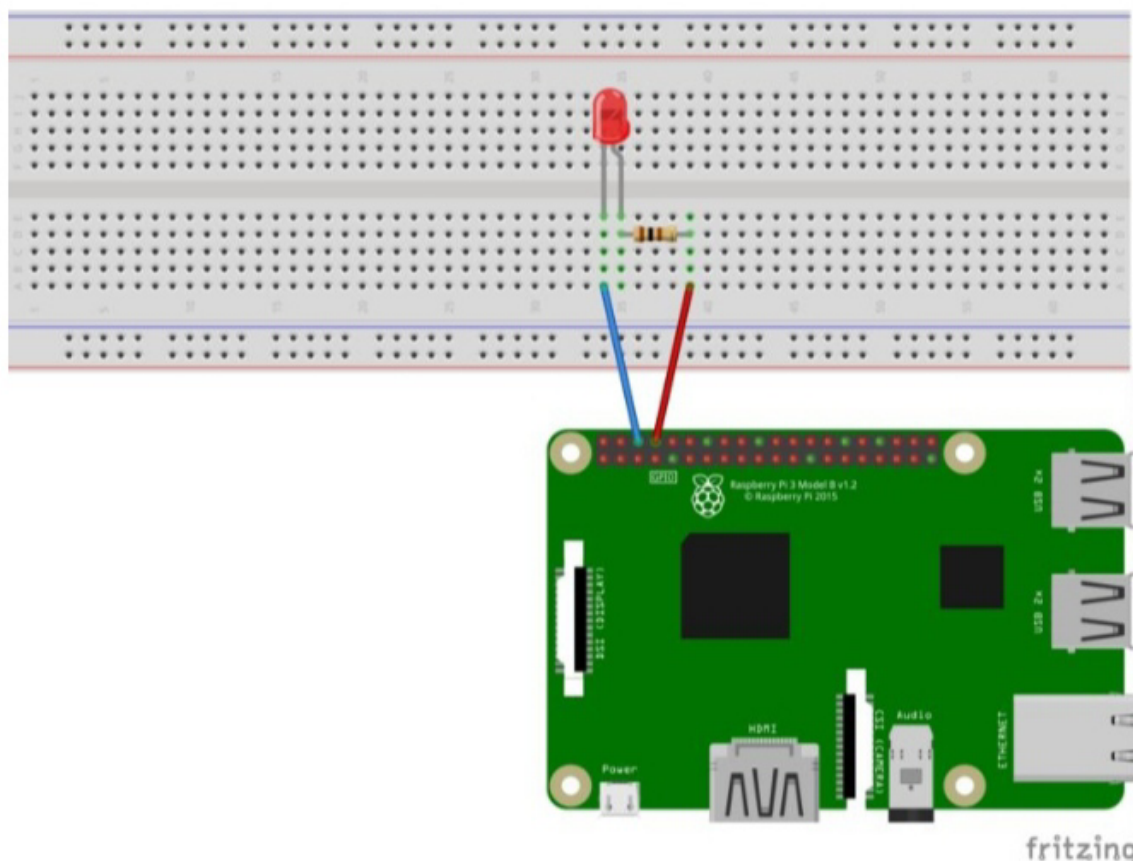With the value calculated for the current limiting resistor we can now hook the LED and resistor up to GPIO pin 8 on the Raspberry Pi. The resistor and LED needs to be in series like the diagram below. To find the right resistor use the resistor color code – for a 100 ohm resistor it needs to be brown-black-brown. You can use your multimeter to double check the resistor value.



When hooking up the circuit note the *polarity* of the LED. You will notice that the LED has a long and short lead. The long lead is the positive side also called the anode, the short lead is the negative side called the cathode. The long should be connected to the resistor and the short lead should be connected to ground via the blue jumper wire and pin 6 on the Raspberry Pi as shown on the diagram.

Writing the Python Software to blink the LED

With the circuit created we need to write the Python script to blink the LED. Before we start writing the software we first need to install the Raspberry Pi GPIO Python module. This is a library that allows us to access the GPIO port directly from Python.

To install the Python library open a terminal and execute the following

```
$ sudo apt-get install python-rpi.gpio python3-rpi.gpio
```

With the library installed now open your favorite Python IDE (I recommend Thonny Python IDE more information about using it [here](#)).

Our script needs to do the following:

- Initialize the GPIO ports
- Turn the LED on and off in 1 second intervals

To initialize the GPIO ports on the Raspberry Pi we need to first import the Python library, the initialize the library and setup pin 8 as an output pin.

second intervals by setting the output pin to either high (on) or low (off). We do this inside a infinite loop so our program keep executing until we manually stop it.

```
while True: # Run forever
    GPIO.output(8, GPIO.HIGH) #
    Turn on
    sleep(1) #
    Sleep for 1 second
    GPIO.output(8, GPIO.LOW) #
    Turn off
    sleep(1) #
    Sleep for 1 second
```

Combining the initialization and the blink code should give you the following full Python program:

```
import RPi.GPIO as GPIO # Import
Raspberry Pi GPIO library
from time import sleep # Import
the sleep function from the time
module

GPIO.setwarnings(False) # Ignore
warning for now
```